
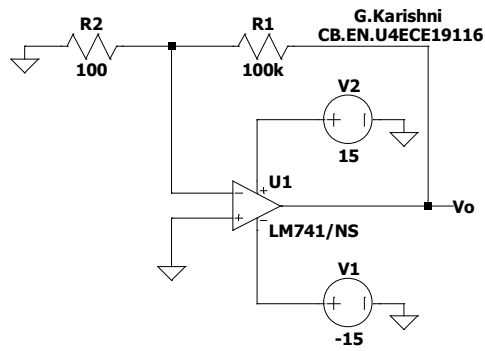


3. Ground Pin 3


a) output for 100k Ω

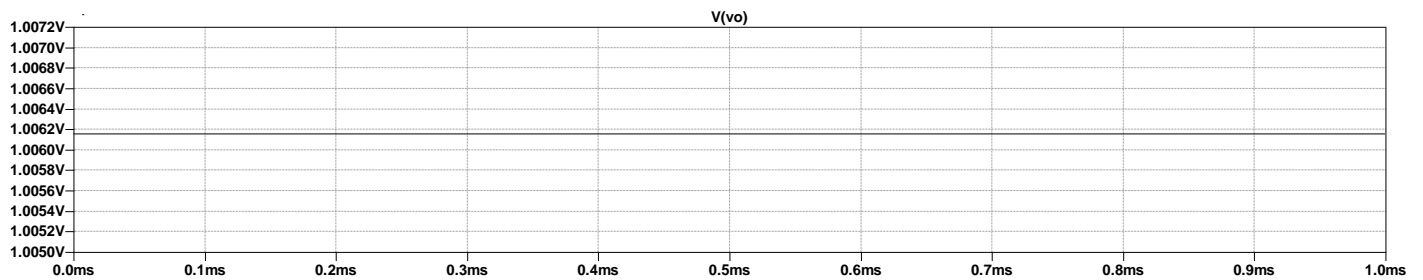


```
.tran 1m  
.include C:\Users\karish\Downloads\snom211\LM741.MOD
```




b) output for 81k Ω

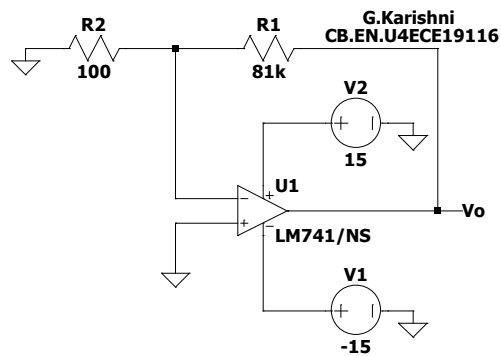

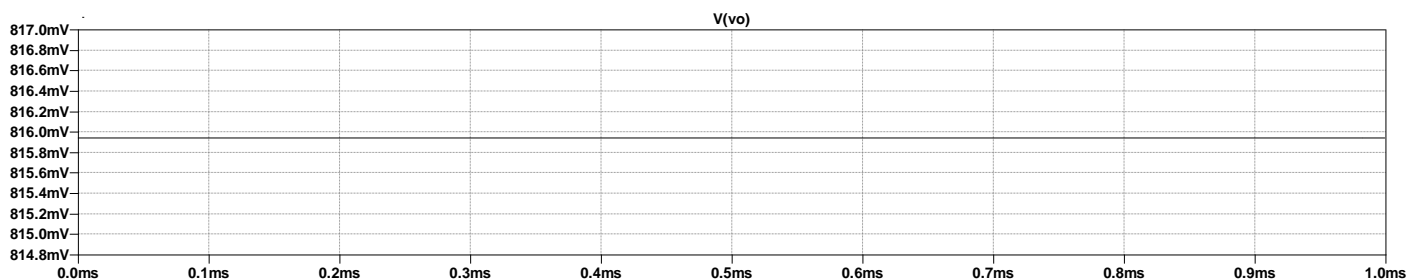
```
.tran 1m  
.include C:\Users\karish\Downloads\snom211\LM741.MOD
```




c) output for 220k Ω

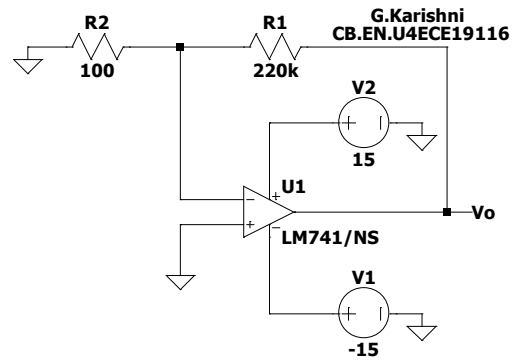

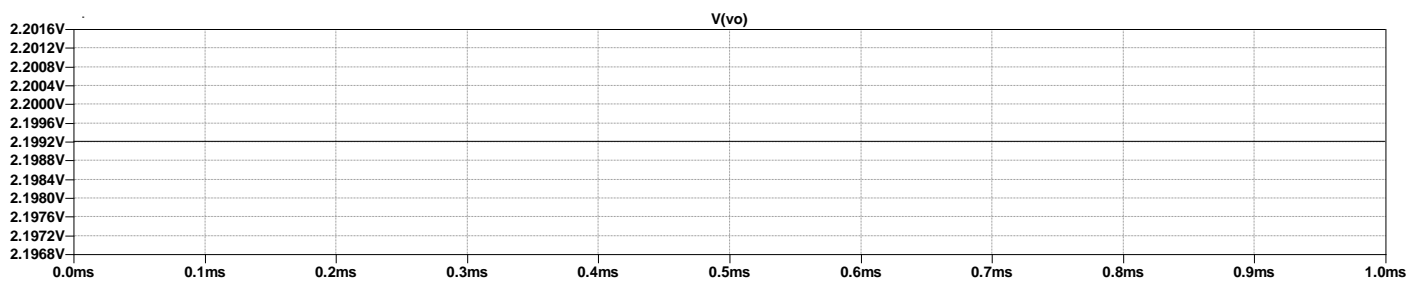
.tran 1m
.include C:\Users\karish\Downloads\snom211\LM741.MOD




d) output for 330k Ω

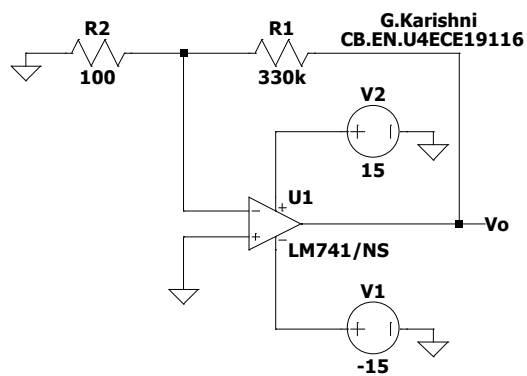

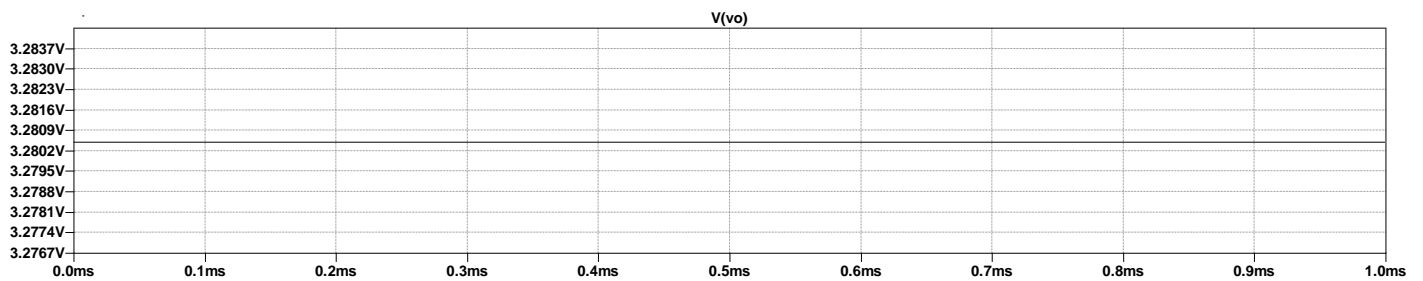
.tran 1m
.include C:\Users\karish\Downloads\snom211\LM741.MOD



e) output for 560k Ω

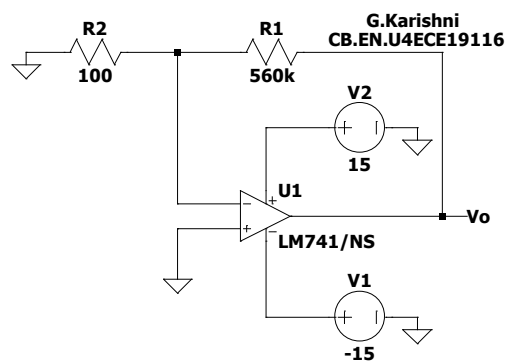

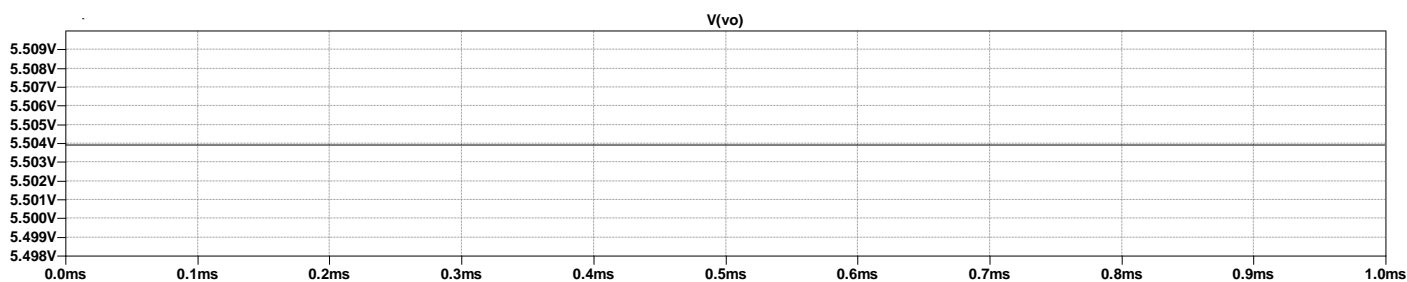
```
.tran 1m  
.include C:\Users\karish\Downloads\snom211\LM741.MOD
```




4. Square wave as input



a) with amplitude as 2V and period 1ms

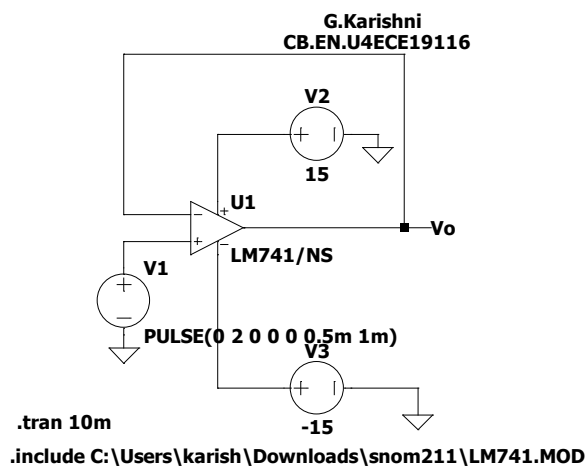

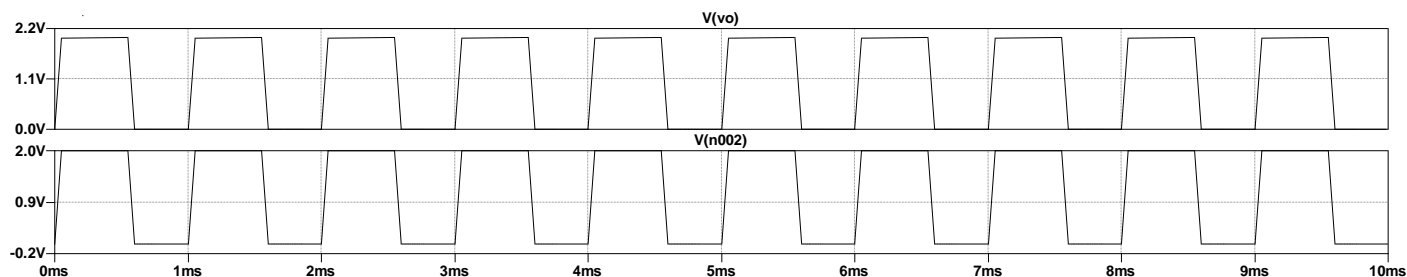
```
.tran 10m  
.include C:\Users\karish\Downloads\snom211\LM741.MOD
```



a) with amplitude as 10V and period 1ms

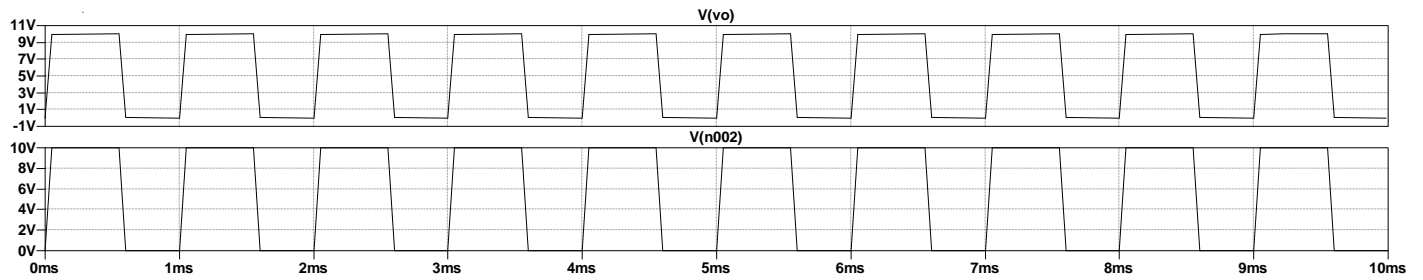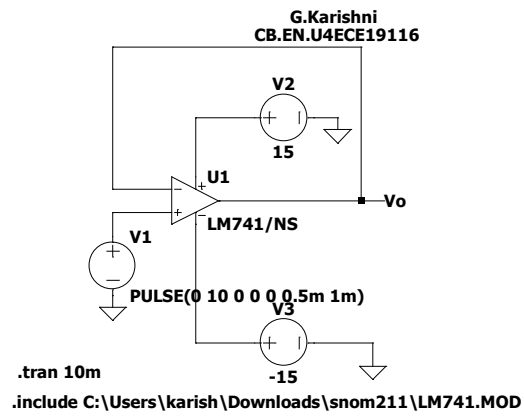

8. Sine wave as input with 20mV

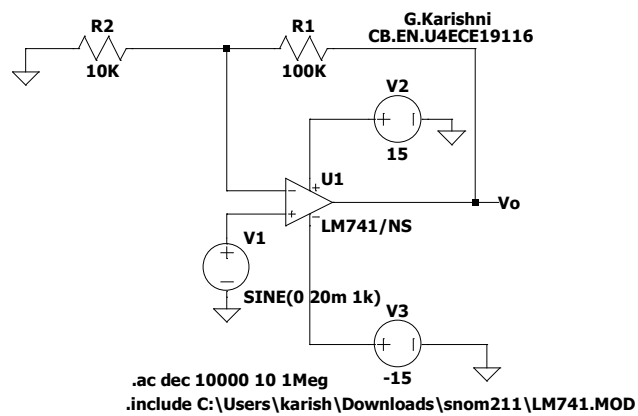

Frequency response

